

# FINAL LAB REPORT


NAME	INDEX NO
W.R.A.N.M.W.RATHNAYAKE	150532E

## LAB TASK


1. design and develop a 6-bit arithmetic unit that can add and subtract integers
2. decode instructions and activate necessary components on the processor
3. design and develop k-way b-bit multiplexers
4. develop and use busses
5. verify their functionality via simulation and on the development board

## SCHEMATIC DIAGRAMS


### 1. REGISTER BANK

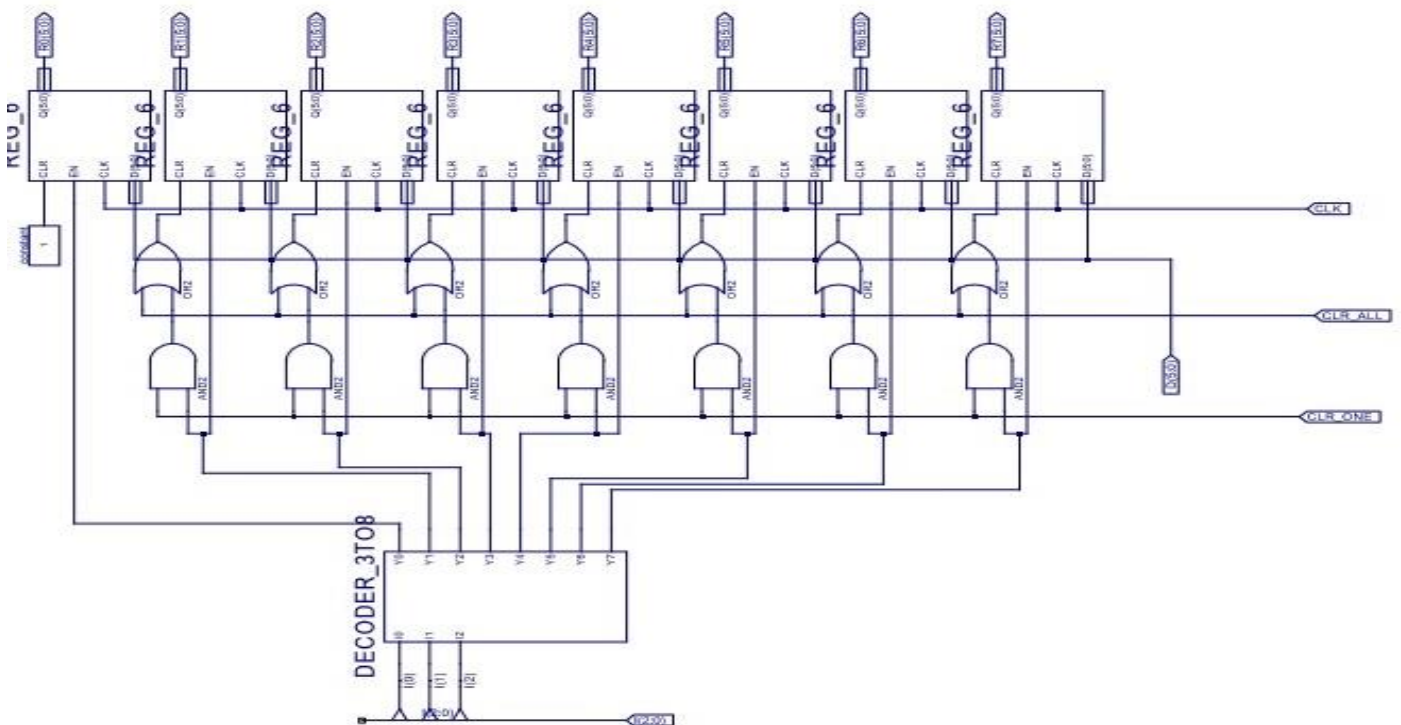


### 2. REGISTER 6 BITS

 


### 3. PROGRAM COUNTER

 


### 4. REGISTER 4 BITS

 


### 5. 4 BIT ADDER FOR COUNTER

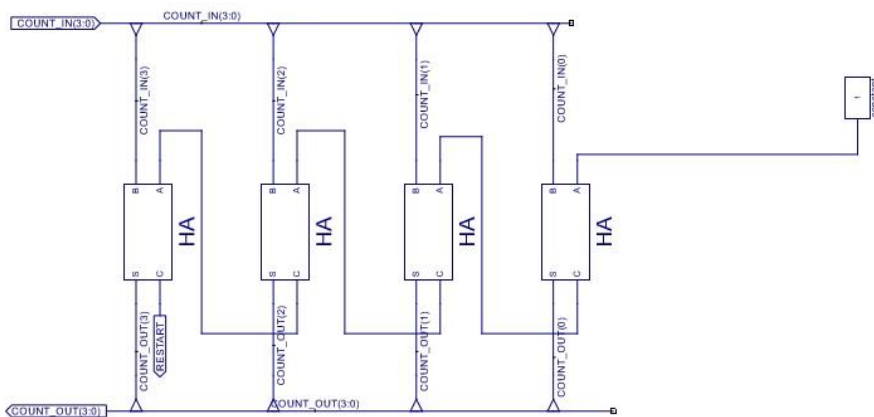

### 6. LUT FOR SEVEN SEGMENT DISPLAY


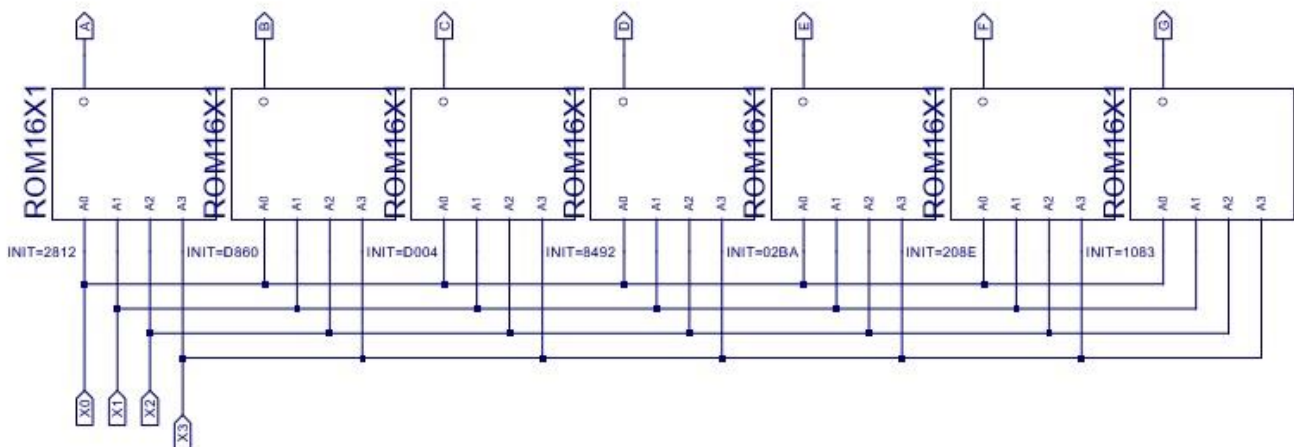


## 7. 6 BITS ARITHMATIC UNIT

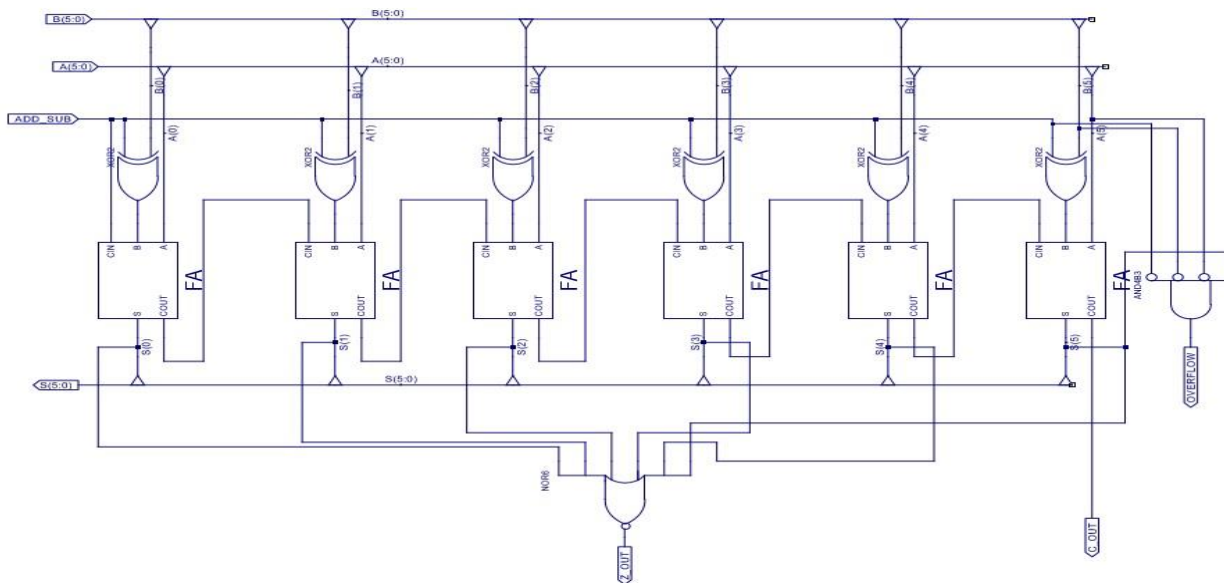


## 8. DECODER 3 TO 8


## 9. MUX 8 TO 1

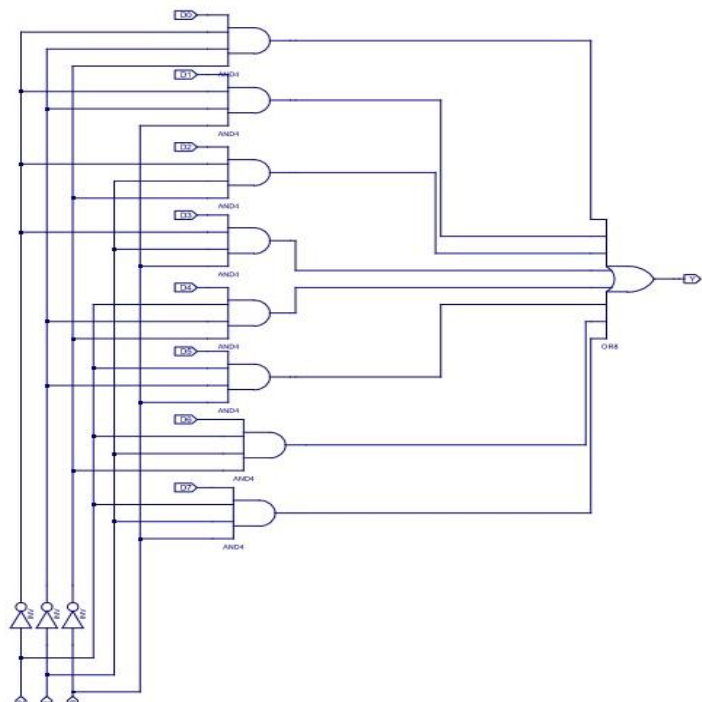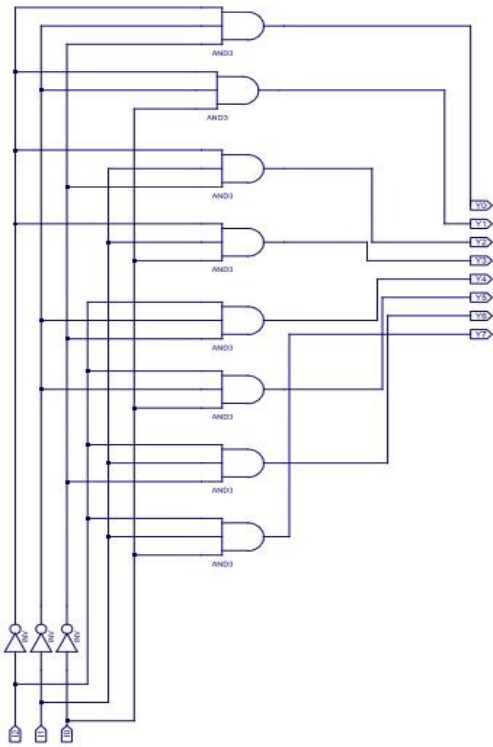


## 10. MUX 2 WAY 4 BITS

 


11. MUX 8 WAT 3 BITS

 


12. MUX 8 WAY 6 BITS

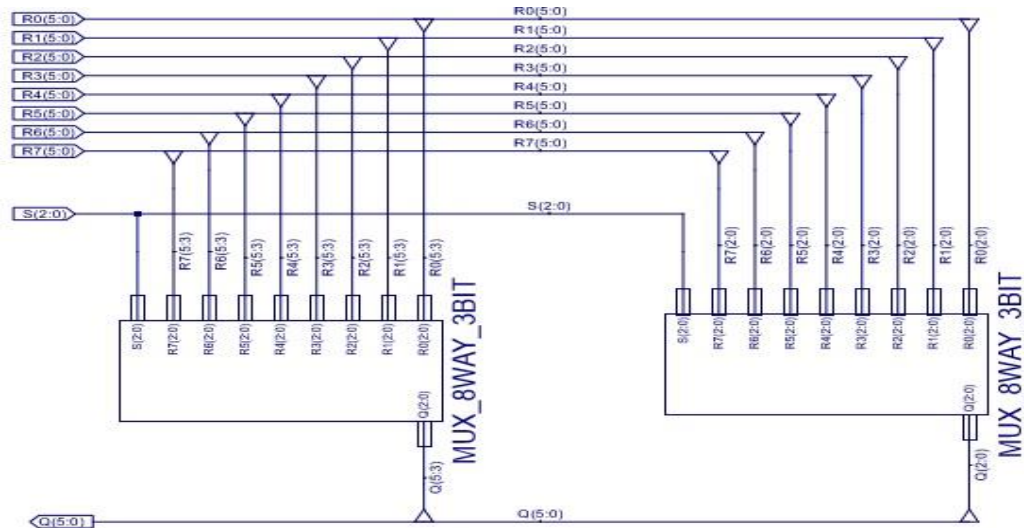

13. MUX UNIT 8 WAY 6 BITS 2

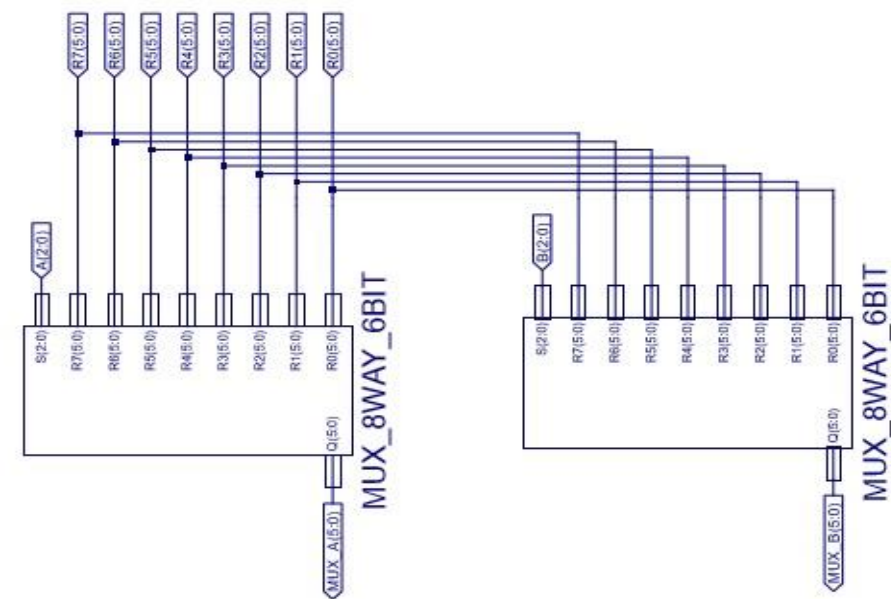

## 14. SEQUENCE GENERATER

 


## 15. BINARY TO DECIMAL CONVERT UNIT 1 VERILOG MODULE

```


23
24 module convert_1(in_A,out_B);
25     input [3:0] in_A;
26     output [3:0] out_B;
27     reg [3:0] out_B;
28
29     always @ (in_A)
30     case (in_A)
31     4'b0000: out_B <= 4'b0000;
32     4'b0001 : out_B <= 4'b0001 ;
33     4'b0010 : out_B <= 4'b0010 ;
34     4'b0011 : out_B <= 4'b0011 ;
35     4'b0100 : out_B <= 4'b0100 ;
36     4'b0101 : out_B <= 4'b1000 ;
37     4'b0110 : out_B <= 4'b1001 ;
38     4'b0111 : out_B <= 4'b1010 ;
39     4'b1000 : out_B <= 4'b1011;
40     4'b1001 : out_B <= 4'b1100;
41     default: out_B <= 4'b0000;
42     endcase
43 endmodule

```

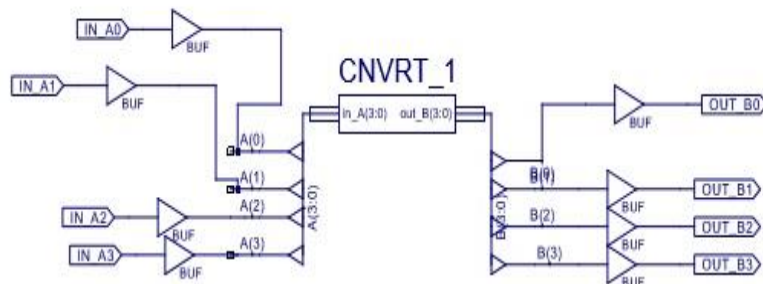


## 16. BIN TO DEC CONVERT
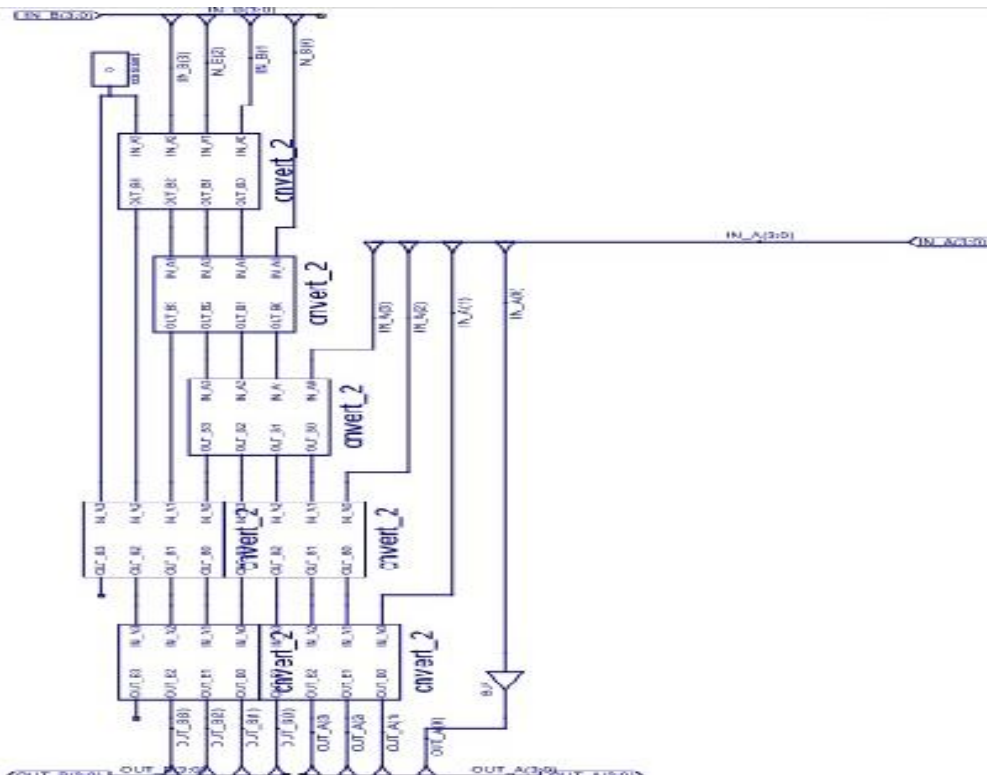
## 17. BIN TO DEC CONVERTER FINAL [8 BITS]






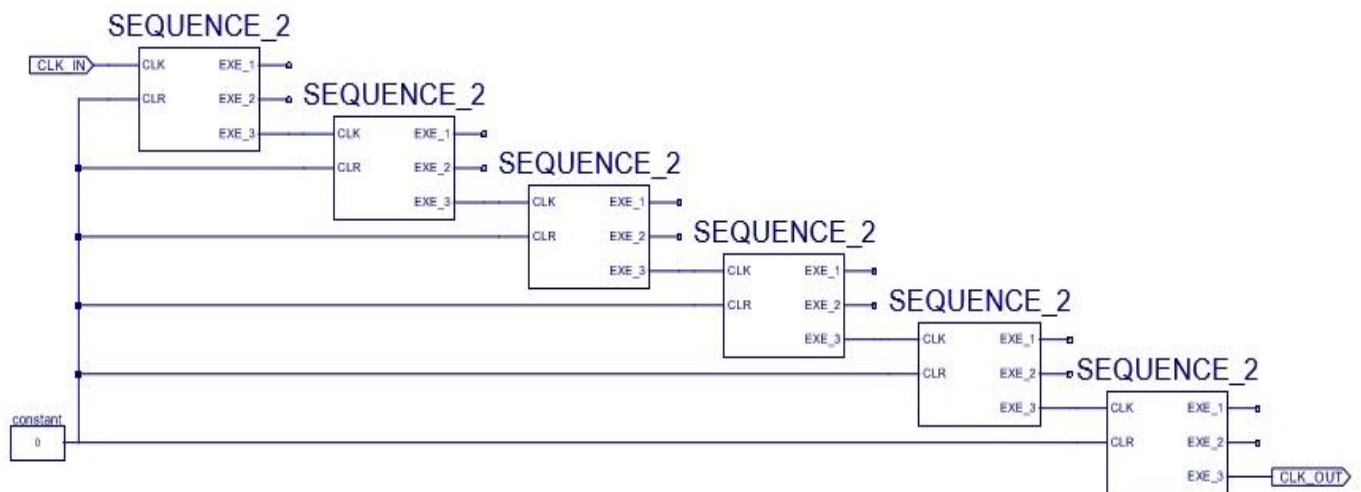
## 18. TIME DELAY MAKER [FD\_DELAY] FOR SEVEN SEGMENTS




## 19. PROGRAM ROM 15 BITS

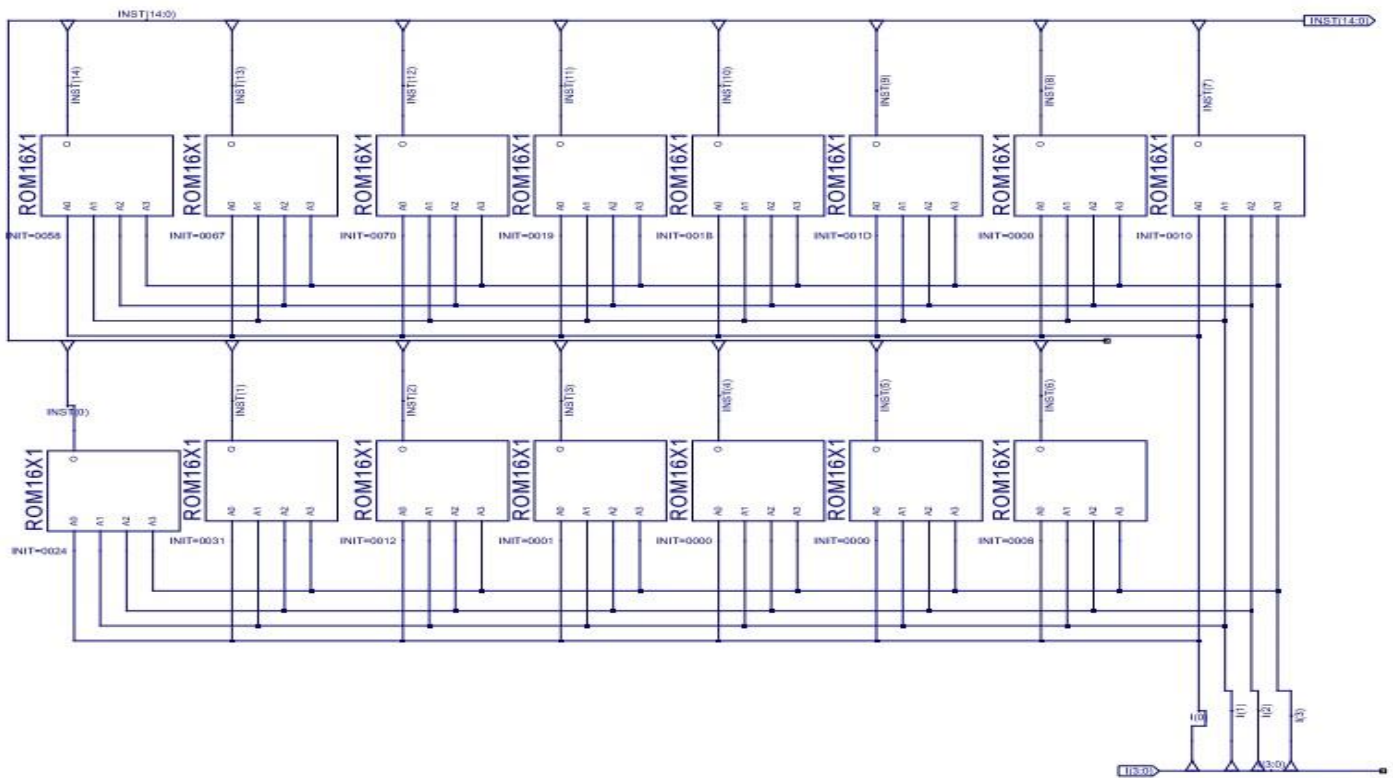


## 20. SEVEN SEGMENT DISPLAY ADAPTER

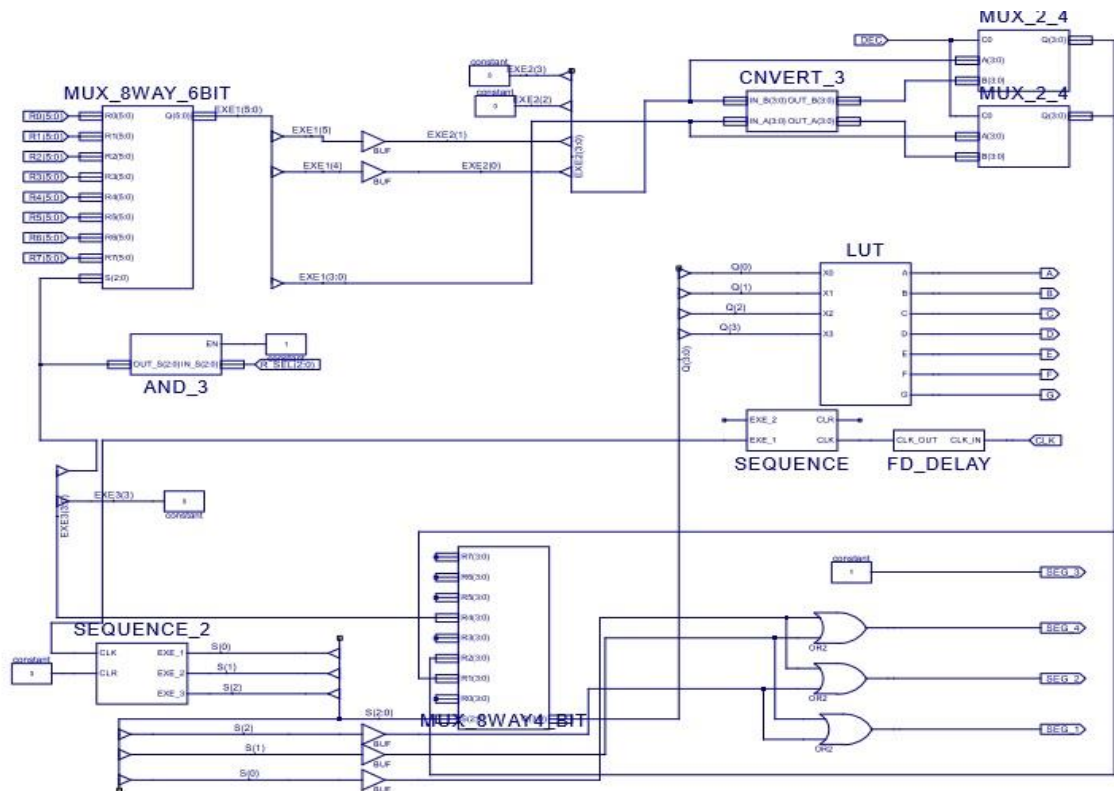


## 21. INSTRUCTION DECODER

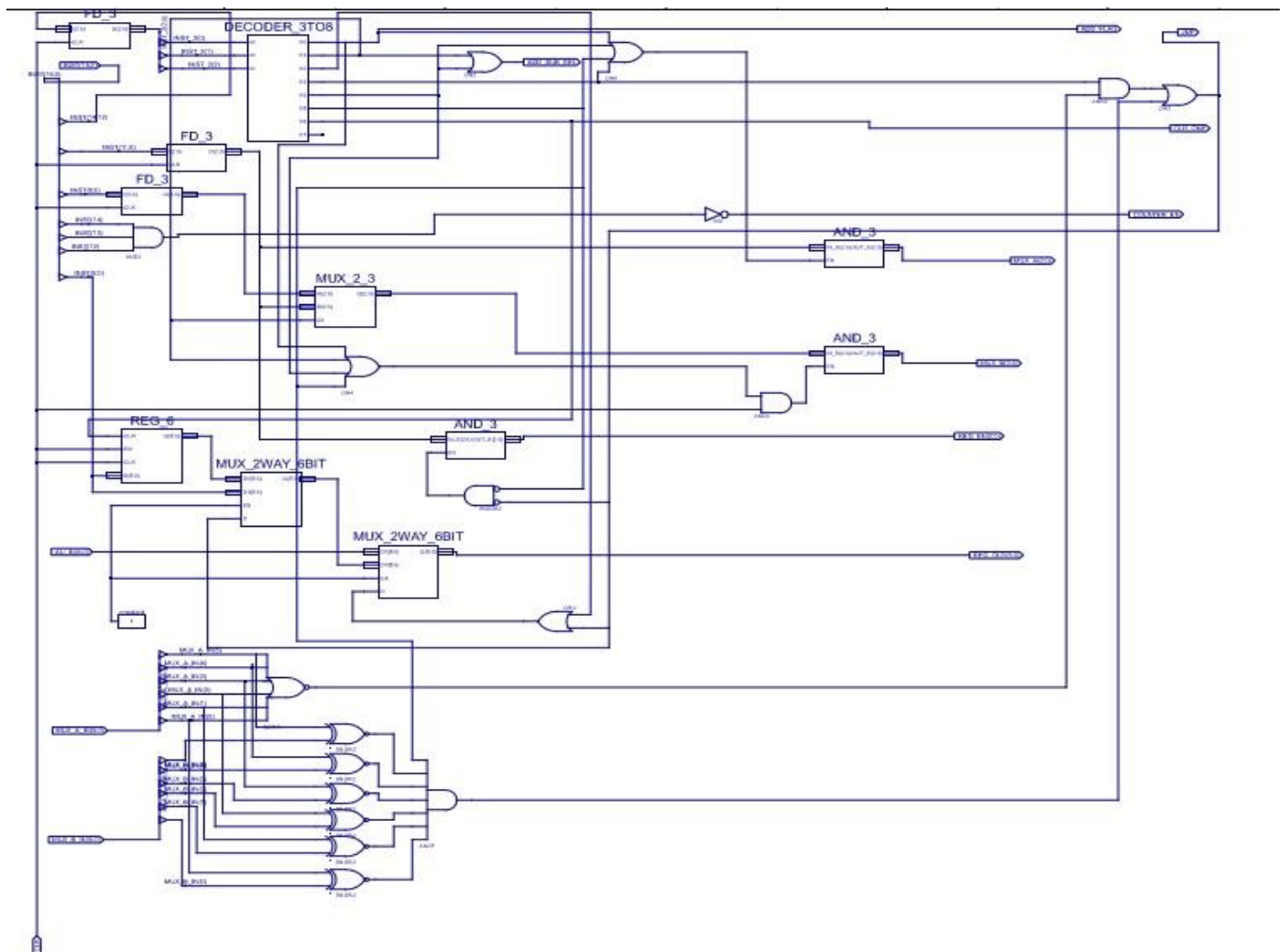

## 22. SYS\_CLOCK SWITCHER

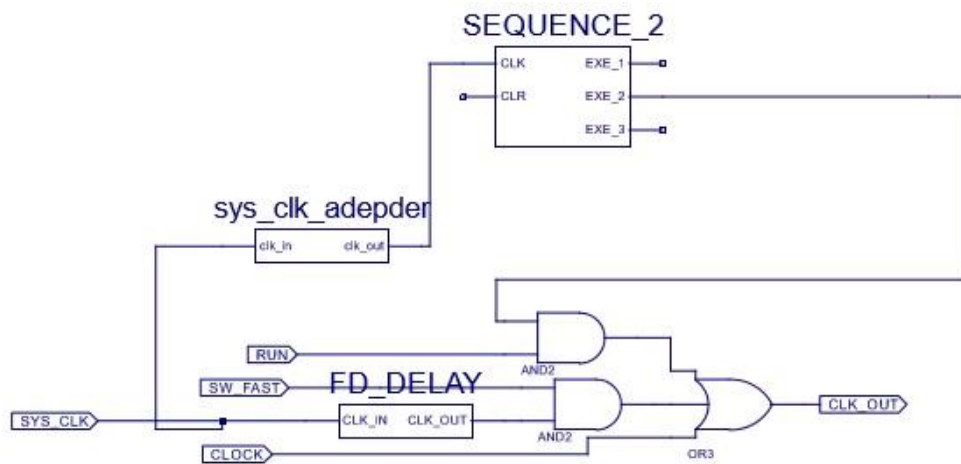


## 23. PROCESSOR FINAL

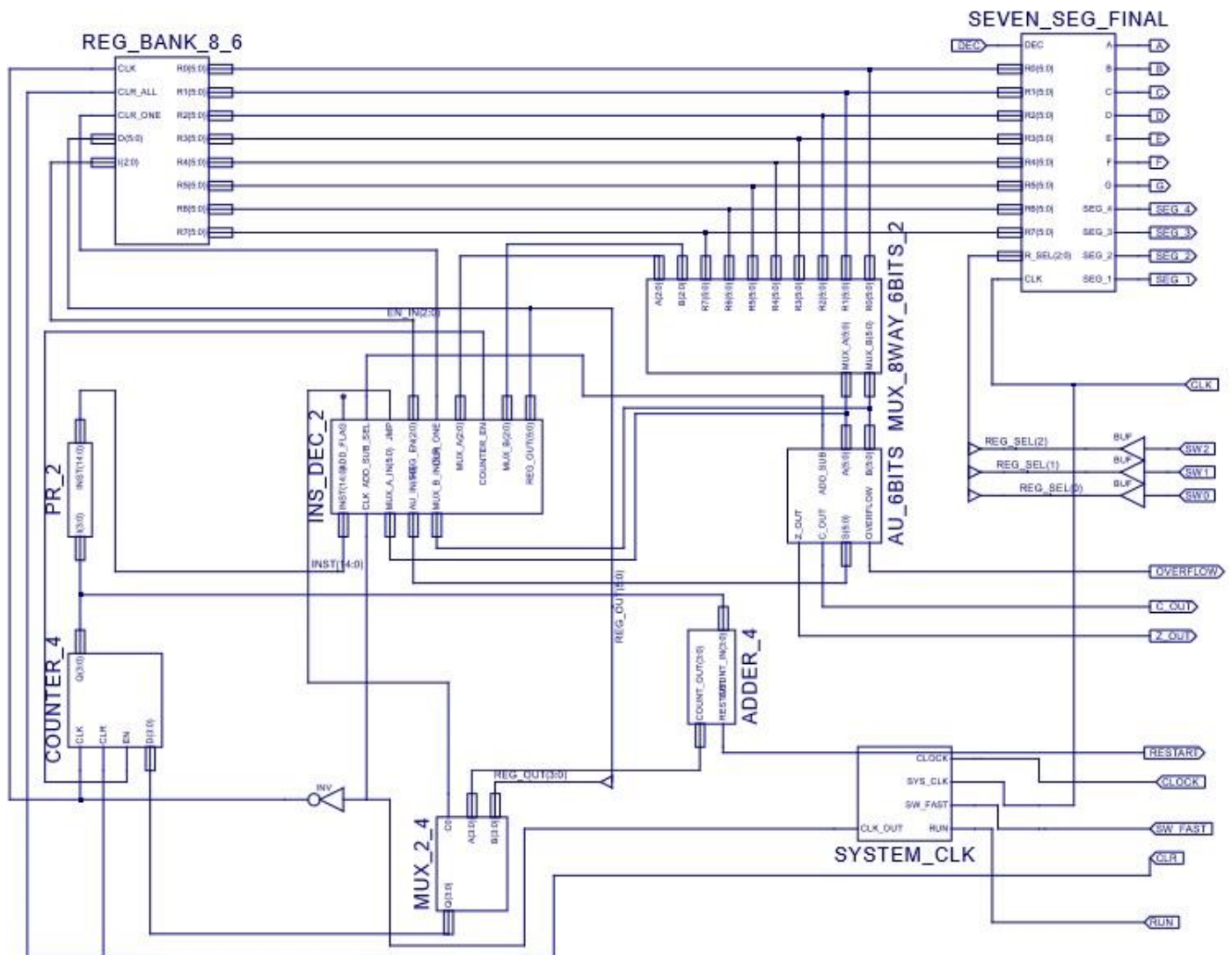




TEST BENCH TIMMING DIAGRAMS


1. DECODER 3 TO 8

 


2. ADDER 4 BITS

 


3. ARITHMETIC UNIT 6 BITS

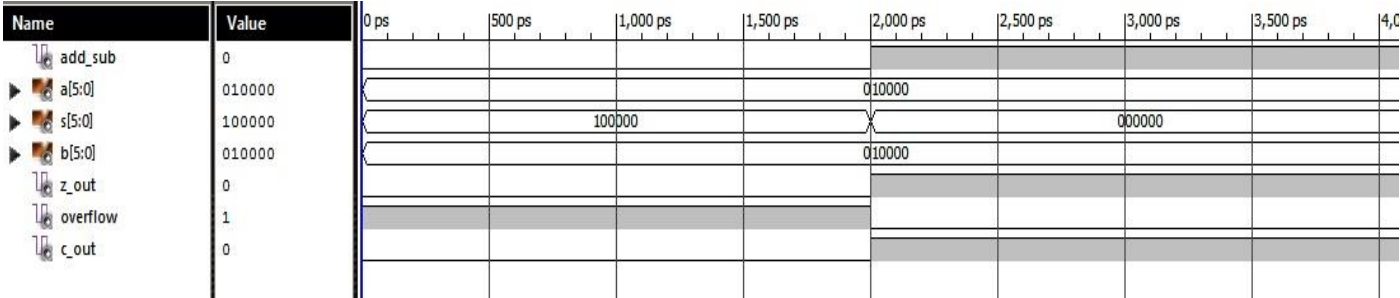


#### 4. BIN TO DEC CONVERTER

 


#### 5. MUX 8 TO 1

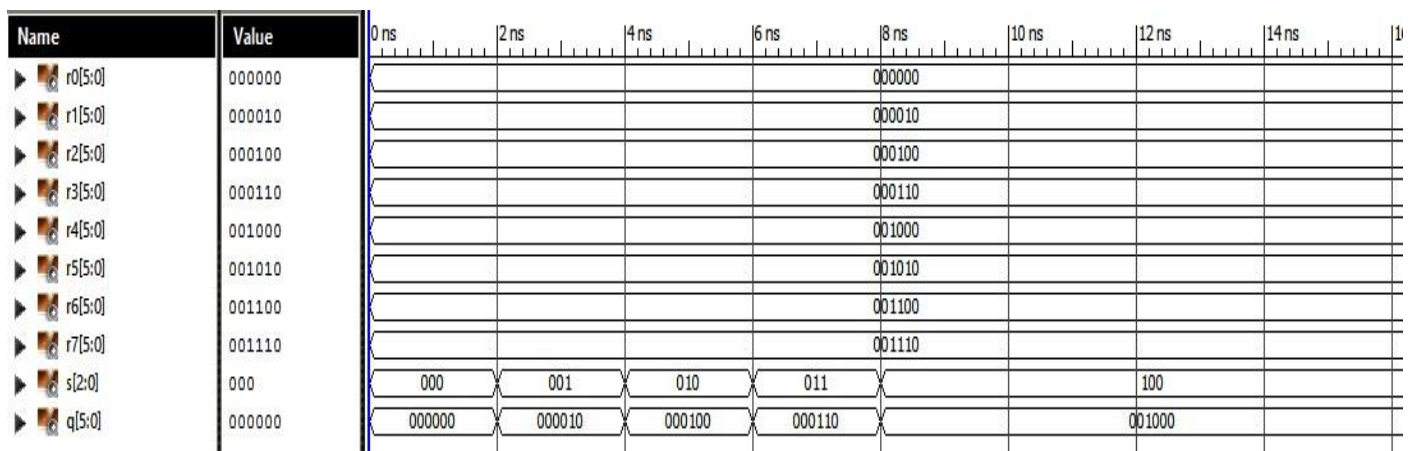


#### 6. PROGRAM ROM

 


#### 7. SEQUENCE GENARATER 1

 


## 8. SEQUENCE GENARETER 2

 

## 9. REGISTER BANK

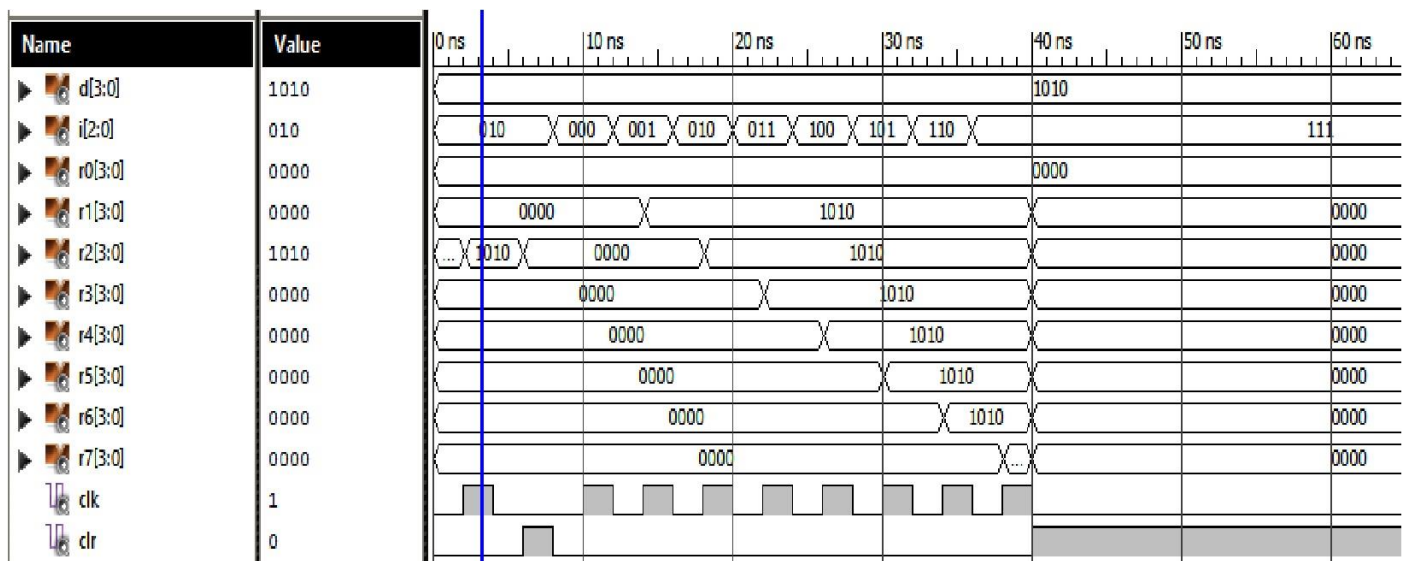

## 10.FINAL 6 BIT PROCESSOR

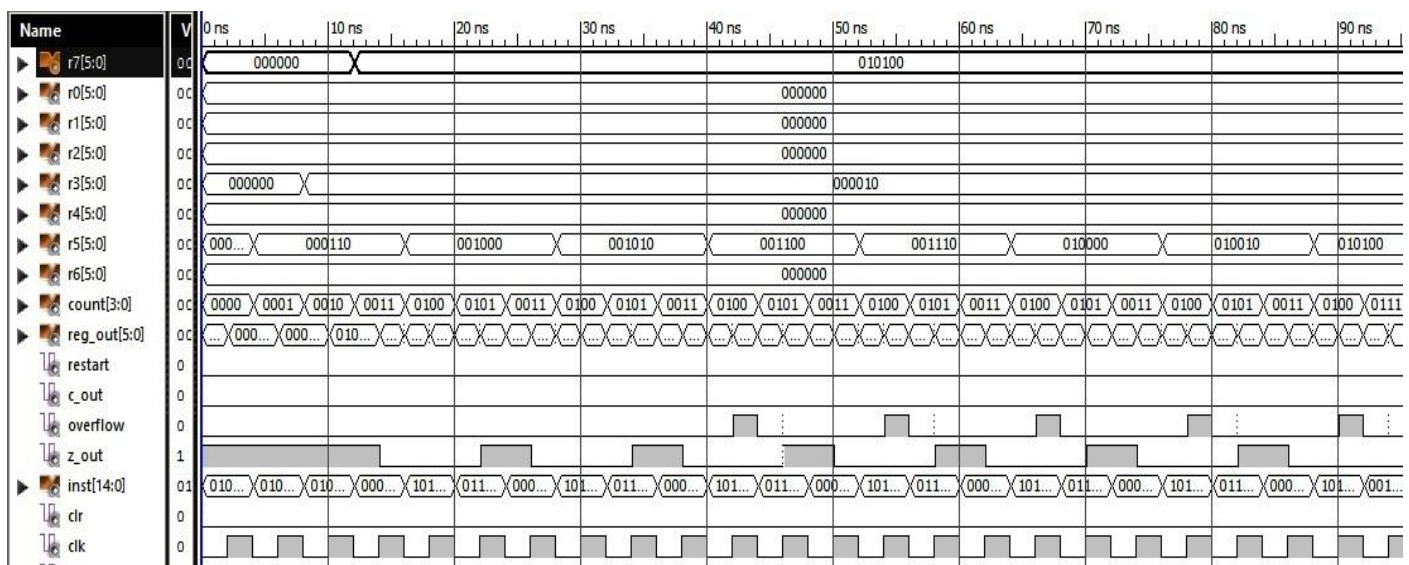

## SIMMULATING ASSEMBLY CODES


### 1. PROGRAM 1

0 - MOVI,R7,10	[0, 1, 0, 1, 1, 1, 0, 0, 0, 0, 0, 1, 0, 1, 0]
1 - MOVI,R2,4	[0, 1, 0, 0, 1, 0, 0, 0, 0, 0, 0, 0, 1, 0, 0]
2 - MOVI,R1,1	[0, 1, 0, 0, 0, 1, 0, 0, 0, 0, 0, 0, 0, 0, 1]
3 - SUB,R7,R1	[1, 0, 0, 1, 1, 1, 0, 0, 1, 0, 0, 0, 0, 0, 0]
4 - COMP,R7,R2,6	[1, 0, 1, 1, 1, 1, 0, 1, 0, 0, 0, 0, 1, 1, 0]
5 - JZR,R0,3	[0, 1, 1, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 1, 1]
6 - END	[1, 1, 1, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0]

### 2. PROGRAM 2

0 - MOVI,R4,10	[0, 1, 0, 1, 0, 0, 0, 0, 0, 0, 0, 1, 0, 1, 0]
1 - MOVI,R3,50	[0, 1, 0, 0, 1, 1, 0, 0, 0, 1, 1, 0, 0, 1, 0]
2 - MOVI,R6,5	[0, 1, 0, 1, 1, 0, 0, 0, 0, 0, 0, 0, 1, 0, 1]
3 - ADD,R4,R6	[0, 0, 0, 1, 0, 0, 1, 1, 0, 0, 0, 0, 0, 0, 0]
4 - COMP,R4,R3,6	[1, 0, 1, 1, 0, 0, 0, 1, 1, 0, 0, 0, 1, 1, 0]
5 - JZR,R0,3	[0, 1, 1, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 1, 1]
6 - END	[1, 1, 1, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0]

## CP-132 BOARD CONFIGURATION

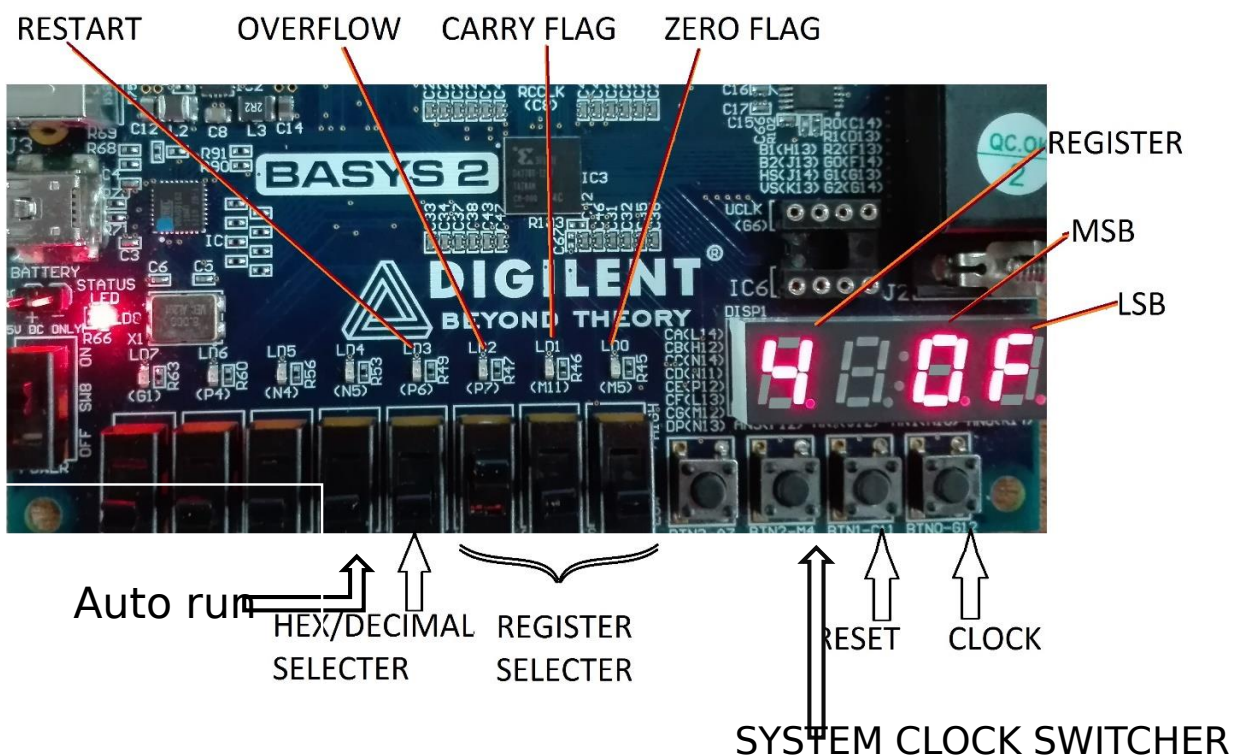

## PROCESSOR SPECIFICATIONS

### 1. SUPPORT 8 INSTRUCTIONS AND 6 BIT REGISTERS

DECODE NUM	INSTRUCTION	INSTRUCTION[14:0]													
		14	13	12	11	10	9	8	7	6	5	4	3	2	1 0
0	ADD	0	0	0	R(A)	R(A)	R(A)	R(B)	R(B)	R(B)	0	0	0	0	0 0
1	NEG	0	0	1	R(A)	R(A)	R(A)	0	0	0	0	0	0	0	0 0
2	MOVI	0	1	0	R(A)	R(A)	R(A)	0	0	0	D	D	D	D	D D
3	JZR	0	1	1	R(A)	R(A)	R(A)	0	0	0	0	0	D	D	D D
4	SUB	1	0	0	R(A)	R(A)	R(A)	R(B)	R(B)	R(B)	0	0	0	0	0 0
5	COMP	1	0	1	R(A)	R(A)	R(A)	R(B)	R(B)	R(B)	0	0	D	D	D D
6	CLR	1	1	0	R(A)	R(A)	R(A)	0	0	0	0	0	0	0	0 0
7	END	1	1	1	0	0	0	0	0	0	0	0	0	0	0 0

1. ADD : ADD REGISTER A AND REGISTER B ,THEN ANSWER GOES TO REGISTER
2. NEG : NEGETION OF REGISTER A SAVE IN ITSELF
3. MOVI : MOVE INTEGER VALUE D UP TO 63 ,MOVES TO REGISTER A
4. JZR : JUMP TO GIVEN D VALUE'TH CODE LINE IF REGISTER A IS ZERO
5. SUB : SUBTRACT REGISTER A FROM REGISTER B ,THEN ANSWER GOES TO REG
6. COMP : JUMP TO GIVEN D VALUE'TH CODE LINE IF REGISTER A IS EQUAL TO RE
7. CLR : CLEAR REGISTER A
8. END : END PROGRAM ,THEN NOTHING CHANGES OCCUR IN SYSTEM WITH CLO  
PULSES

2. WORK TO INTEGER VALUES UP TO 63 WITH 6 BIT AU AND REGISTERS
3. DISPLAY EXACT REGISTER VALUE HEXA DECIMAL OR DECIMAL CORRECTLY
4. ABILITY TO CHECK ALL REGISTER VALUES ON SEVEN SEGMENT DISPLAY BY SWITHING S
5. CONVERT ANY ANSWER TO DECIMAL BY SW 4
6. ALL INSTRUCTIONS ARE RUN WITH EXACT ONE CLOCK PULSE
7. ABILITY TO EXECUTE 16 CODE LINES BY THE USAGE OF 4 BIT ADDER
8. ABILITY TO OBSERVE ZERO, CARRY OUT, OVERFLOW BY FLAGS LED[0,1,2]
9. SWITCH TO SYSTEM CLOCK ONCE AND EXECUTE THE CODE HIGH FAST PUSHING BTN 2
- 10.SWITCH TO AUTORUN PROCEDURE BY SW 5.



## CONCLUSIONS

1. WE CAN DEVELOP A SIMPLE NANO PROCESSOR BY THE COMBINATION OF BASIC LOGIC FLOP, AND ROM S.
2. CLOCK OF THE SYSTEM CAN BE OVERWRITE TO A PUSH BUTTON SWITCH
3. THERE EXISTS CONSIDERABLE DELAY OF LOGIC GATES IN COMBINATIONS THAT EFFECT CIRCUIT TIMMING
4. BY USING GATED CLOCK TO DIFFER THE TIMING OF VARIOUS ELEMENTS OF CIRCUIT, WE CAN MANAGE THE ELEMENTS DELAY
5. VERY HIGH FREQUENCY OF SIMULATING BOARD IS COULDN'T DIRECTLY USE FOR A MULTIPLE SEVEN SEGMENTS AND MAIN EXECUTION.
6. USAGE OF FLIP-FLOPS TO REDUCE SYSTEM CLOCK RATE IS THE METHOD OF SYSTEM CLOCK
7. THE GATES, FLIP-FLOPS, ROM S, AND INPUT OUTPUT MARKERS OF SIMULATING BOARD ARE LIMITED
8. SYSTEM PUSH BUTTONS CAN DEVELOP MORE THAN ONE CLOCK PULSE FOR AN ONE PULSE